


Module - 4

Boost Converter :

- It is also called as boost regulator
- If the input voltage is fixed and the output voltage is greater than the input voltage.

$$V_o > V_s$$

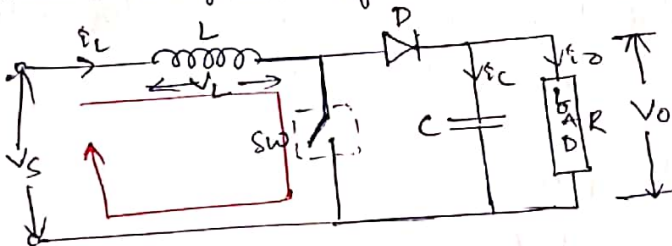- Circuit diagram of boost converter as shown in figure.




- The boost converter has two modes of operation.

Mode I : Switch is ON, diode is OFF

- When switch is ON, (at $t=0$), the input current rises and flow through the inductor.

$$V_L = V_s$$

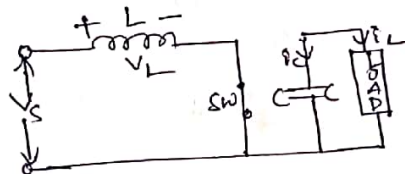

- charging of inductor increases, capacitor is discharged ($V_c \downarrow$)
- Boost convert in steady state operation for this mode using KVL,

$$V_L = V_s$$

$$V_c = L \frac{di_L}{dt} = V_s$$


$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{\Delta T} = \frac{V_s}{L}$$

Since the switch is closed for a time $T_{ON} = \Delta T$ we can say that

$$(\Delta i_L)_{closed} = \left(\frac{V_s}{L}\right) \Delta T$$

Mode II : Switch is OFF, diode ON.

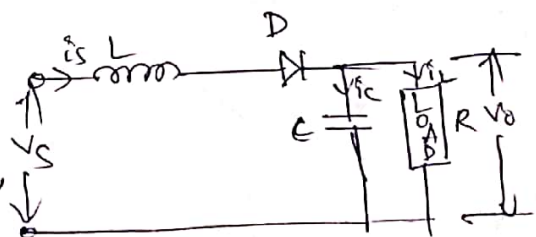- When the switch is OFF at $t=t_1$ Here current flows through the L, C, load and diode.



- the energy stored in inductor is discharged through load.

$$V_L = V_s - V_o$$

- Inductor discharges i_L decreases, capacitor charges so V_c increases.

- Boost converter in steady state operation for mode II using KVL

$$V_s = V_L + V_o$$

$$V_L = V_s - V_o = L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_s - V_o}{L}$$

- Since the switch is open for a time $T_{OFF} = T - T_{ON} = T - dT = (1-D)T$, we can say that $\Delta t = (1-D)T$

$$(\Delta i_L)_{open} = \frac{(V_s - V_o)(1-D)T}{L}$$

- It is already established that the net change of the inductor current over any one complete cycle is zero.

$$(\Delta i_L)_{closed} + (\Delta i_L)_{open} = 0$$

$$\left(\frac{V_s}{L}\right) dT + \left(\frac{V_s - V_o}{L}\right)(1-d)T = 0$$

$$\left(\frac{V_s}{L}\right) dT = -\left(\frac{V_s - V_o}{L}\right)(1-d)T$$

~~$V_s d + (V_s - V_o)(1-d) = 0$~~
 ~~$V_s d - V_s + V_o = V_o(1-d)$~~
 ~~$V_s d - V_s + V_o = V_o - V_o d$~~
 ~~$V_s d - V_s + V_o + V_o d = V_o$~~
 ~~$V_s d - V_s + V_o(1+d) = V_o$~~
 ~~$V_s d - V_s + V_o = V_o(1-d)$~~

$$V_s d = -(V_s - V_o)(1-d)$$

$$V_s d = (-V_s + V_o)(1-d)$$


$$V_s d = -V_s + V_o + V_s d - V_o d$$

$$V_s d + V_s + V_o - V_s d + V_o d = 0$$

$$V_s + V_o + V_o d$$


$$V_s = V_o(1-d)$$

$$V_o = \frac{V_s}{1-d}$$

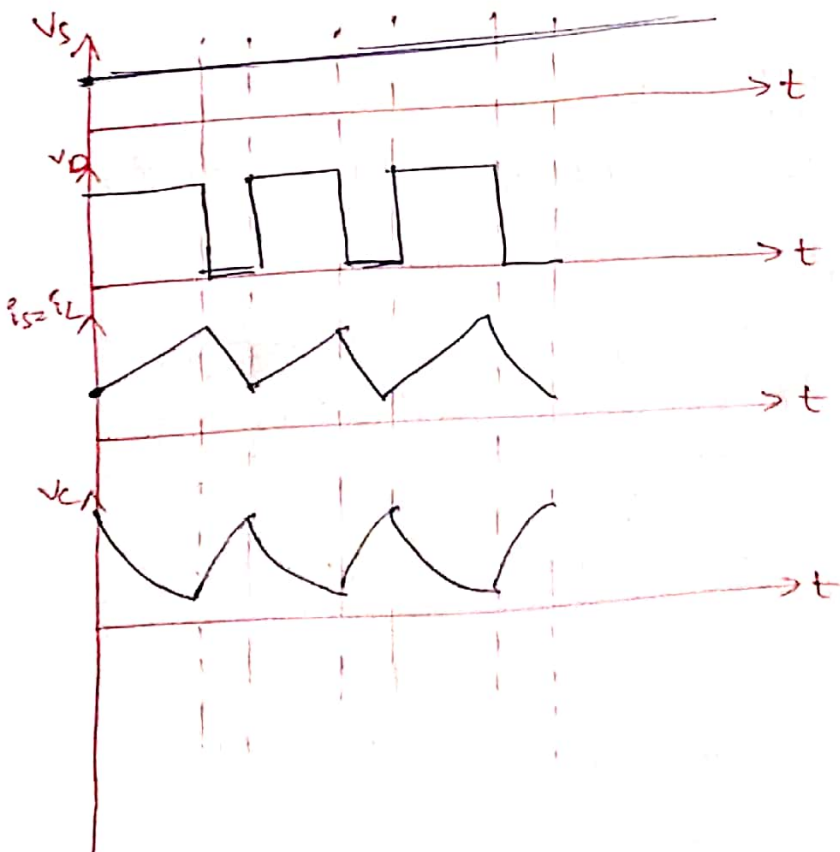


Buck-Boost Converter / Regulator.

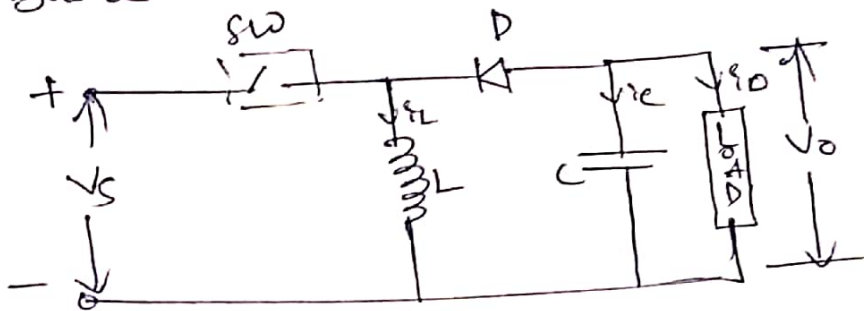- It is a combination of two converters, which can perform either of two functions.
- The polarity of output voltage is opposite to that of the input voltage.
- This is also called as inverting or fly wheel regulator
- Circuit diagram of Buck-Boost Converter is shown in figure.



- It operates in two modes.

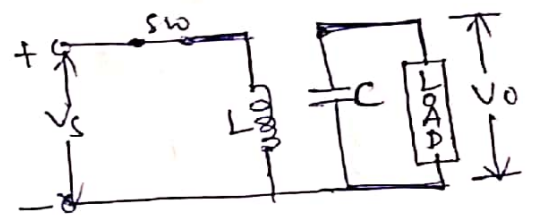- Mode I: Switch is on, Diode OFF
- When switch is on, current flows through the inductor
 - L is charging i_L increases



$$V_L = V_S$$

- Buck boost converter in steady state operation for this mode


- using KVL $V_S = V_L = L \frac{di_L}{dt} = V_S \Rightarrow \frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{dT} = \frac{V_S}{L}$

- Since the switch is closed for a time $T_{on} = dT$, we can say that $dT = \Delta t$.

$$(\Delta i_L)_{closed} = \left(\frac{V_S}{L}\right) dT \quad \text{--- } \textcircled{1}$$

Mode II: Switch is OFF, Diode on

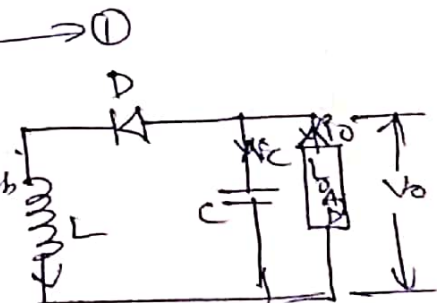- When switch is off, the current passes through the load and capacitor.



→ The energy stored in inductor is transferred to load.

$$V_L = -V_O$$

- Buck boost converter in steady state operation for mode II using KVL

$$\therefore v_L = -V_0$$

$$L \frac{di_L}{dt} = -V_0$$

$$\frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{-V_0}{L}$$

- Since the switch is open for a time $T_{OFF} = T - T_{ON} = T - dT = (1-d)T$ we can say $\Delta t = (1-d)T$

$$(\Delta i_L)_{open} = \left(\frac{-V_0}{L} \right) (1-d)T \longrightarrow \textcircled{2}$$

$$(\Delta i_L)_{closed} + (\Delta i_L)_{open} = 0$$

$$\left(\frac{V_s}{L} \right) dT + \left(\frac{-V_0}{L} \right) (1-d)T = 0$$

$$\left(\frac{V_s}{L} \right) dT = \frac{V_0}{L} (1-d)T = 0$$

$$V_s d = V_0 - V_0 d$$

$$\boxed{V_0 = \frac{V_s d}{1-d}}$$

waveforms: